

State Diagram :

- State Tables: show relation between i/p's, o/p's, p.s. and n.s.

↳ used for building state diagram

P.S	i/p's	N.S	o/p's
Q_1, Q_2, \dots	X_1, X_2, \dots	Q_{n+1}, Q_{n+2}, \dots	Y_1, Y_2, \dots
0 0		
0 0 ... 1			

- A sequential circuit can contain memory elements \rightarrow latches and flip-flops

One can determine number of state in the state diagram from total number of memory elements. (depend what type of memory you using).

Specific case: Let say a seq. circuit only contains two D flip flops

1 flip flop has two state : 0 and 1 (for Q)

$$2^2 = 4$$

For seq. circuit only contains flip-flops with only Q and \bar{Q}


$$\text{number of states} = 2^n \leftarrow \# \text{ of FF.}$$

A FF can be represent by a diagram with no o/p.

↳ just p.s, inputs and n.s.


Example SS. for a JK FF.

Chara. Table.	Q_n	J	K	Q_{n+1}	
	0	0	0	0	a JK FF only has two states \leftarrow state 0. $\begin{cases} S_0 = 0 \\ S_1 = 1 \end{cases}$ \uparrow state 1
	0	0	1	0	
	0	1	0	1	
	0	1	1	0	
	1	0	0	1	
	1	0	1	0	
	1	1	0	1	
	1	1	1	0	

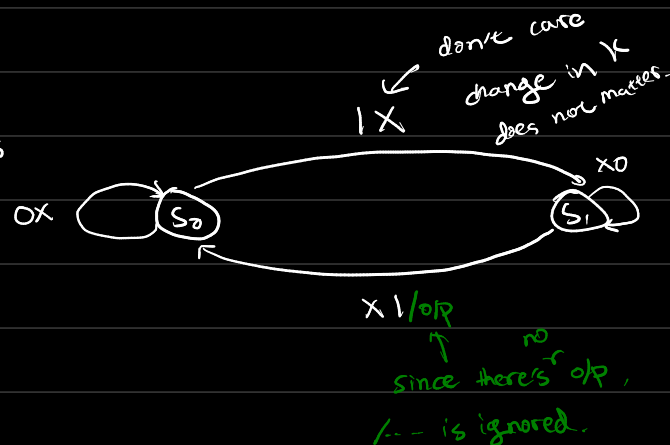

$$\begin{array}{ccc} \text{State Eq.} & LMS & = RMS \\ & \uparrow & \\ & Q_{n+1} & \text{P.S \& I/P} \end{array}$$

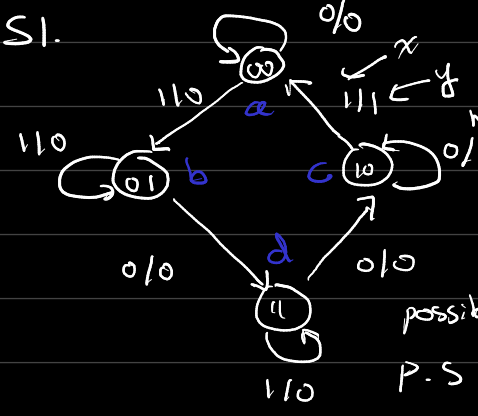Designed Procedure for Clocked Seq. Circuits with Example



S2. State table :-

		N.S.		Output (y)	
		x=0	x=1	x=0	x=1
	P.S.	$Q_A^+ Q_B^+$		$Q_A^+ Q_B^+$	
		Q_A	Q_B		
0	0	0	0	0	0
0	1	1	1	0	0
1	0	1	0	1	1
1	1	1	0	0	0

the possible n.s after transition from each p.s when input x is 0 is 1
o/p for each p.s → n.s when x=0

S3. Check the next state and o/p.

→ if the next state and o/p for two p.s are the same → this example is not possible.

S4. Assign state to the equivalent binary code

a = 00
b = 01
c = 10
d = 11
if each state is assigned to something other than binary code.

S5. 4 states → 2 FFs

of FF → $2^n = \# \text{ of states}$

letter symbol
↓
first FF → Q_A
second FF → Q_B

S6. implementation dependence. (This case T-FF)

S7. Excitation Table

P.S.

Q_A	Q_B	x	Q_A^+	Q_B^+	T_A	T_B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	1	1	0	0
0	1	1	0	1	0	0	0
1	0	0	1	0	0	0	1
1	0	1	0	0	1	0	1
1	1	0	1	0	0	1	0
1	1	1	1	1	0	0	0

FF: 1/2

obtain through n.s. truth table and * excitation table

Are FF being used.


clk	T	Q_{n+1}
0	x	Q_n
1	0	Q_n
1	1	$\overline{Q_n}$

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

S8. $T_A = \overline{Q_A} Q_B \overline{x} + Q_A \overline{Q_B} x$ Use k-map

$T_B = \overline{Q_A} \overline{Q_B} x + Q_A Q_B \overline{x}$ if necessary.

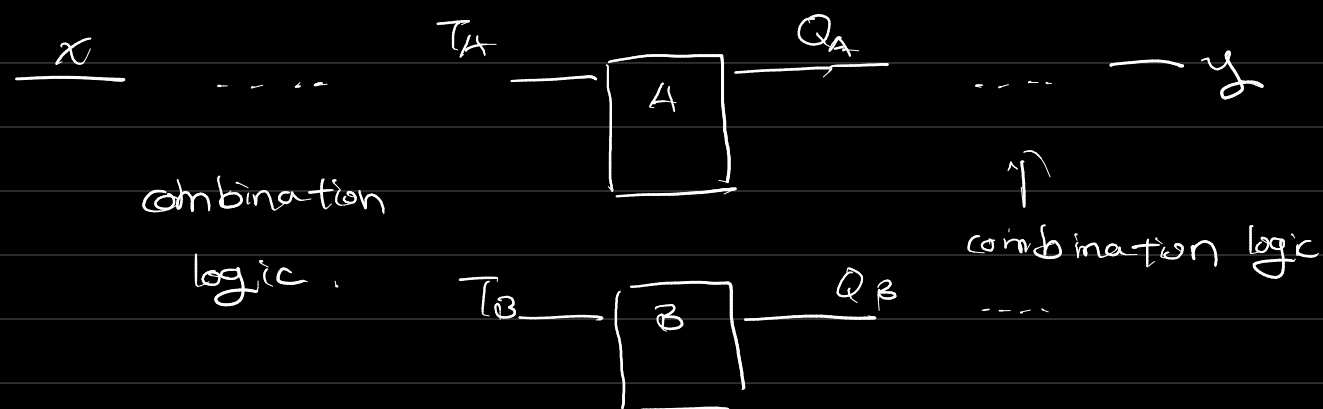$y = Q_A \overline{Q_B} \overline{x} + Q_A \overline{Q_B} x$




Moore's Circuit (Moore State Machine).


o/p's only depend on p.s.

$$\text{Ex: } Y = \bar{Q}_A + Q_B$$


↑ ↗
output of FF.

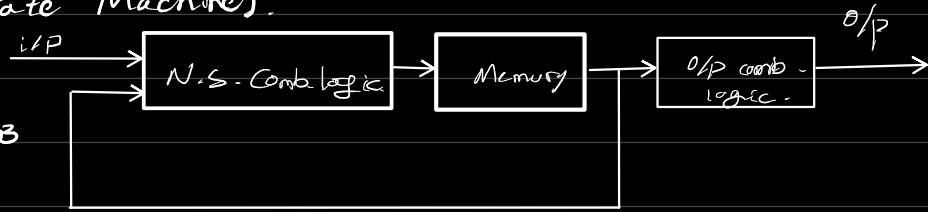

Moore State Diagram (random Example)

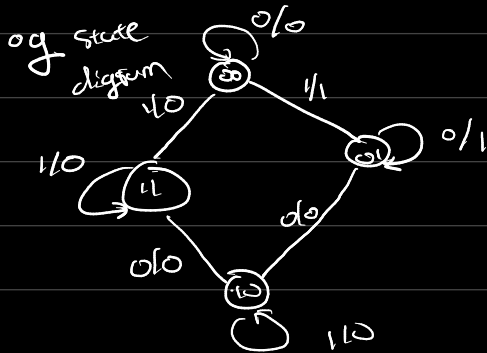

Moore's version

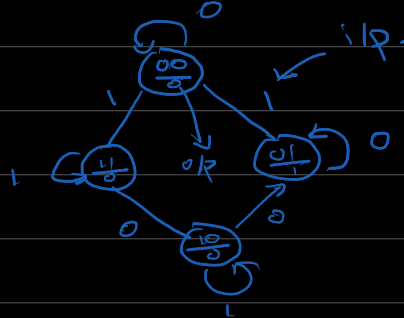

Mealy State Machine

o/p depend on p.s. and i/p.

